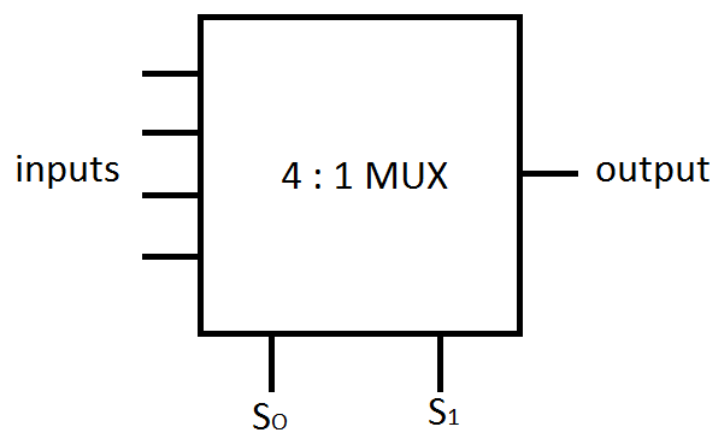


**Military Institute of Science and Technology (MIST)**  
**Department of Computer Science and Engineering**  
**CSE-315 (DSD Sessional)**  
**CSE-14, Level-3, Term-II**  
**Lab-01(Group-A+B)**

1. Implement 4:1 MUX in Circuit Maker software and simulate it.

**Instructions:**

- a. Use basic gates (AND, OR and inverter)
- b. Use Logic switch and logic display to give input and output.



2. Software implementation of 4-bit combinational logic shifter using basic gates and Shifter IC.

$S_0$	$S_1$	$S_2$	Operation	Function
0	0	0	$F \leftarrow A$	Transfer A to F
0	0	1	$F \leftarrow A'$	Complement of A
0	1	0	$F \leftarrow \text{shr } A$	Shift right A into F
0	1	1	$F \leftarrow \text{shl } A$	Shift left A into F
1	0	0	$F \leftarrow \text{cr } A$	Circular right A into F
1	0	1	$F \leftarrow \text{cl } A$	Circular left A into F
1	1	0	$F \leftarrow \text{All } 0\text{'s}$	Transfer 0's into F
1	1	1	$F \leftarrow \text{All } 1\text{'s}$	Transfer 1's into F

**F:** 4-bit outputs (F0, F1, F2, F3)  
**A:** 4-bit inputs (A0,A1,A2,A3)  
**S:** 3-bit Selection variables (S0, S1, S2)